

Wang-LeGrand-Lab1-326

Helena Wang, Benjamin LeGrand

TA: Aden Briano

September 28-29, 2025

We both contributed equally when performing both parts of the regular assignment, the extra credit assignment, and the lab report.

High Level Circuit

 


Figure 1: High Level Circuit Schematic

On a high level the switch and button inputs enter the logic unit. The logic unit decides what operation what must be performed and outputs the result to result-po[7:0]. This signal travels the IsevenSegDisplay module and where the result is interpreted and displayed via interfacing with the display pins. In addition result-po[7:0] drives controls the LEDs. The clkdiv module provides a slower clock to the seven segment display and the increment module assists the logic unit in its increment function.

Logic Unit

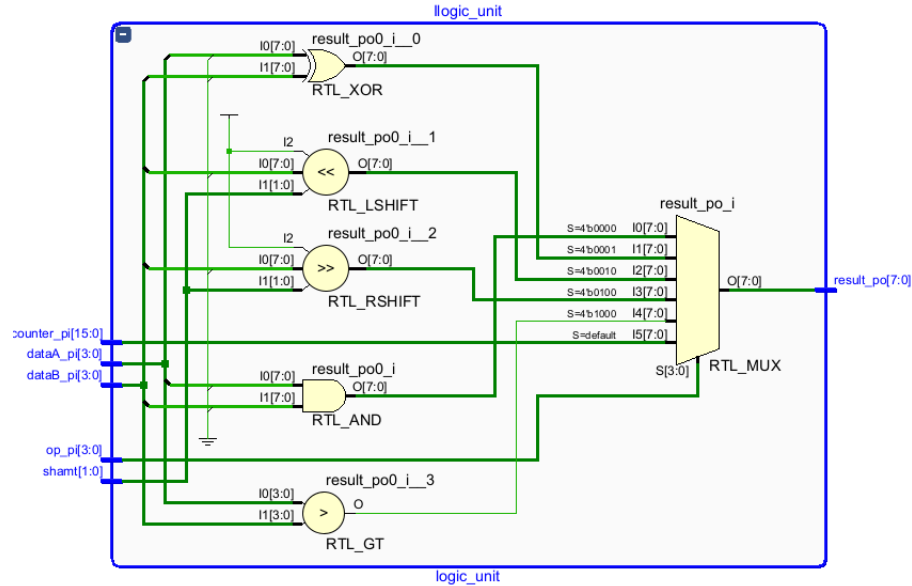


Figure 2: Logic Unit Schematic

Signals from the clock counter, switch, and buttons flow into the Logic Unit. `op_pi[3:]` is determined by single button presses and decides the operation performed with `dataA_pi[3:0]` and/or `dataB_pi[3:0]`. The output is stored in `result_po[7:0]`, which holds the values to be displayed before being interpreted by the seven segment display.

Extra Credit [10 points]: Parity Checker

To implement the parity checker, we computed `p_en` and `p_val` in `logic_unit.v`. `p_en` is an enable signal representing whether or not we want to display the parity, and `p_val` stores the actual parity. In top, we passed these values to the `sevenSegDisplay` module called `IsevenSegDisplay`. Then in `sevenSegDisplay`, we passed `p_en` and `p_val` to the `segmentFormatter` modules along with a bus to specify the relative position of each formatter in order to correctly display the EVEN or ODD text.